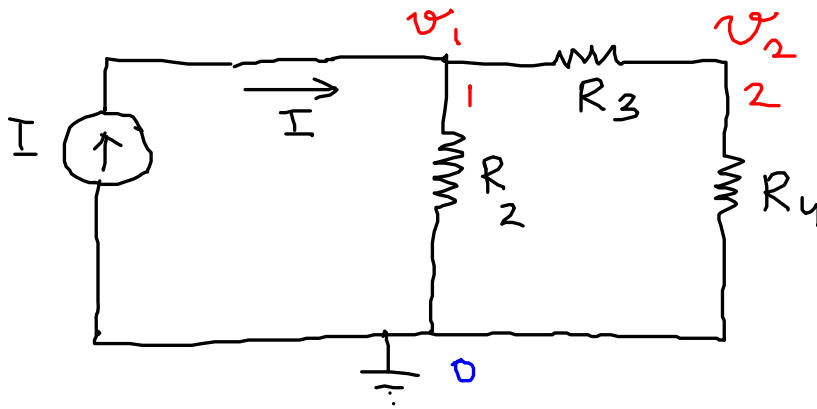


$$\text{KCL 1: } \frac{V - v_1}{R_1} + \frac{0 - v_1}{R_2} + \frac{v_2 - v_1}{R_3} = 0$$

$$\text{KCL 2: } \frac{v_1 - v_2}{R_3} + \frac{0 - v_2}{R_4} = 0$$

two equations in two unknowns



$$\text{KCL 1: } I + 0 - \frac{v_1}{R_2} + \frac{v_2 - v_1}{R_3} = 0$$

Two equations
two unknowns

$$\text{KCL 2: } \frac{v_1 - v_2}{R_3} + 0 - \frac{v_2}{R_4} = 0$$


Total number of unknown node voltages

$$= n - 1 - m$$

total # of nodes

ground (known)

of voltage sources

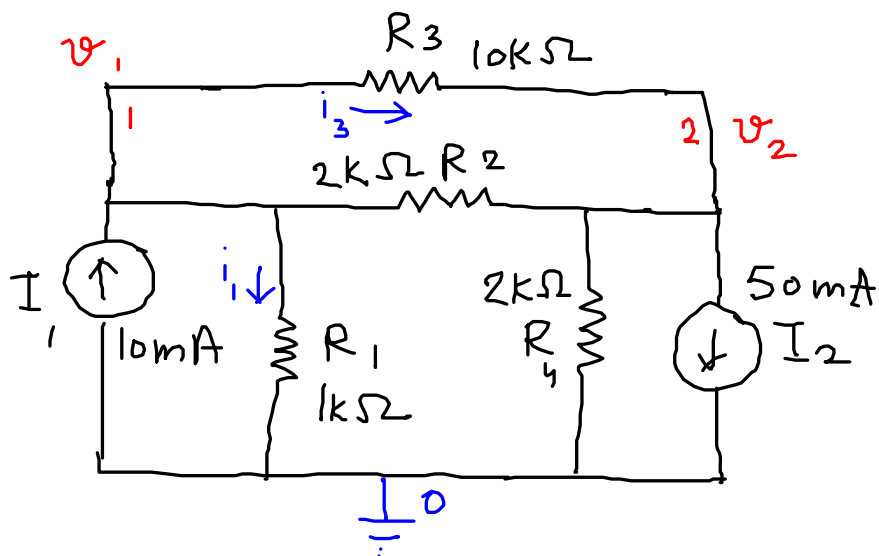


$$1: 10\text{mA} + \frac{v_2 - v_1}{10\text{k}\Omega} + \frac{v_2 - v_1}{2\text{k}\Omega} + \frac{0 - v_1}{1\text{k}\Omega} = 0$$

$$2: -50\text{mA} + \frac{v_1 - v_2}{10\text{k}\Omega} + \frac{v_1 - v_2}{2\text{k}\Omega} + \frac{0 - v_2}{2\text{k}\Omega} = 0$$

$$v_1 = -13.57\text{V} \quad v_2 = -52.86\text{V}$$

$$i_1 = \frac{v_1 - 0}{1\text{k}\Omega} = -13.57\text{mA}$$
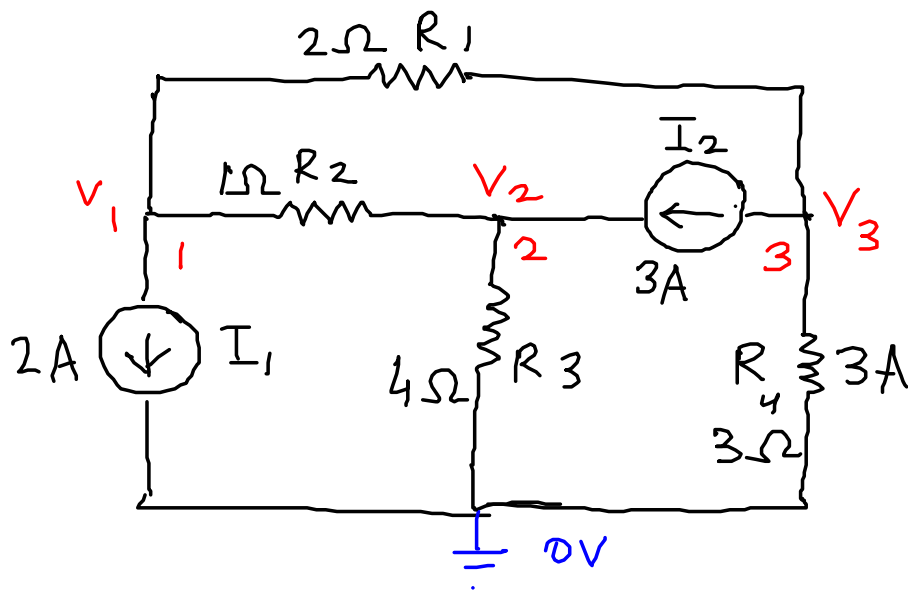
$$i_3 = \frac{v_1 - v_2}{10\text{k}\Omega} = \frac{-13.57 + 52.86}{10\text{k}} = 3.93\text{mA}$$




$$1: -2A + \frac{V_2 - V_1}{1\Omega} + \frac{V_3 - V_1}{2\Omega} = 0$$

$$2: 3A + \frac{V_1 - V_2}{1\Omega} + \frac{0 - V_2}{4\Omega} = 0$$

$$3: -3A + \frac{V_1 - V_3}{2\Omega} + \frac{0 - V_3}{3\Omega} = 0$$

solution
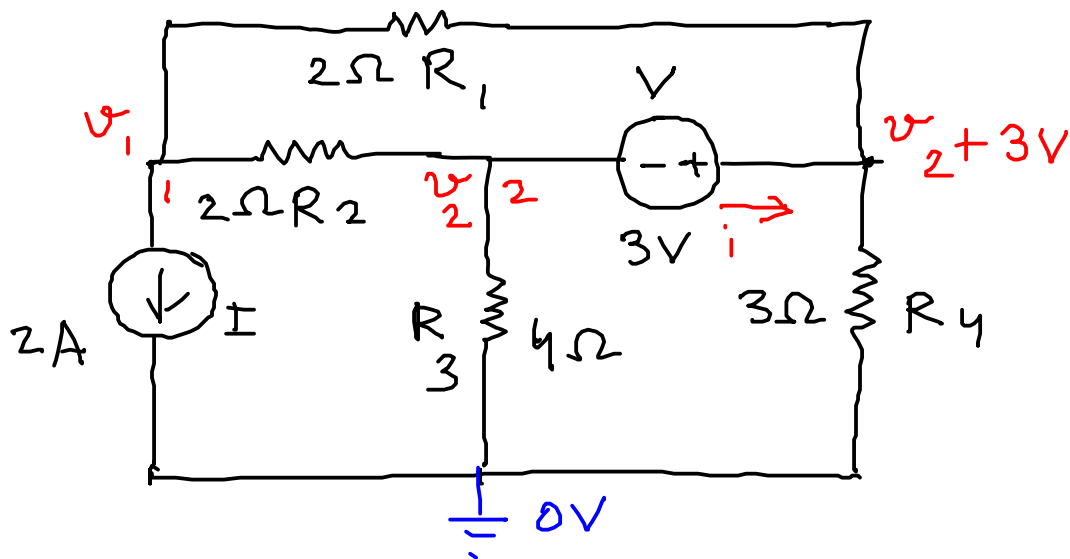
$$v_1 = -3.5V \quad v_2 = -0.4V \quad v_3 = -5.7V$$



$$1: -2 + \frac{v_2 - v_1}{2\Omega} + \frac{v_2 + 3V - v_1}{2\Omega} = 0$$

$$2: \frac{v_1 - v_2}{2\Omega} + \frac{0 - v_2}{4\Omega} - i = 0$$


$$3: i + \frac{v_1 - v_2 + 3V}{2\Omega} + \frac{0 - v_2 - 3V}{3\Omega} = 0$$

solution

$$v_1 = -5.64V$$


$$v_2 = -5.14V$$

$$i = 1.04A$$

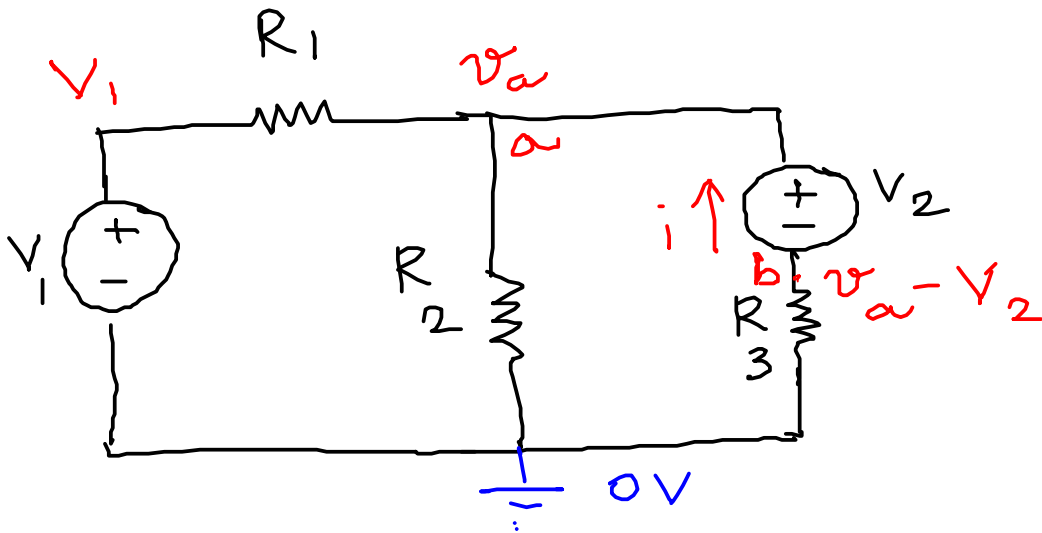


$$a: \frac{V_1 - V_a}{R_1} + \frac{0 - V_a}{R_2} + i = 0$$

$$-i + \frac{0 - V_a + V_2}{R_3} = 0$$

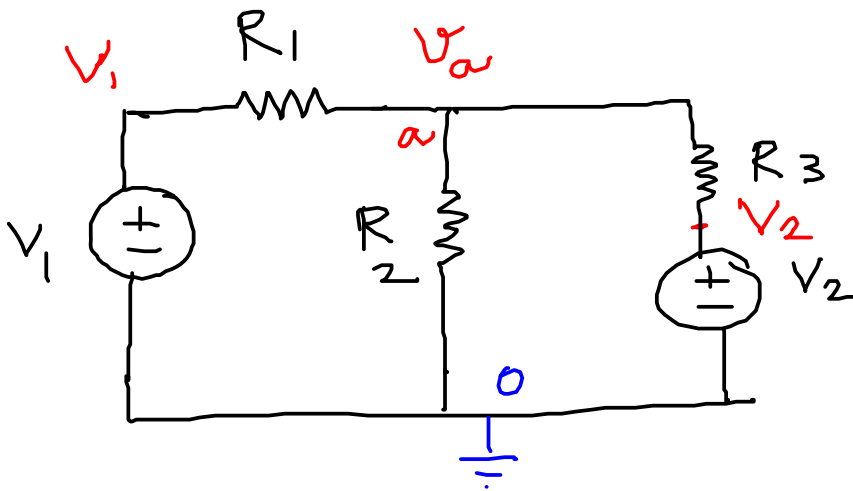

$$a: \frac{V_1 - V_a}{R_1} + \frac{0 - V_a}{R_2} + \frac{V_2 - V_a}{R_3} = 0$$


one unknown, one equation

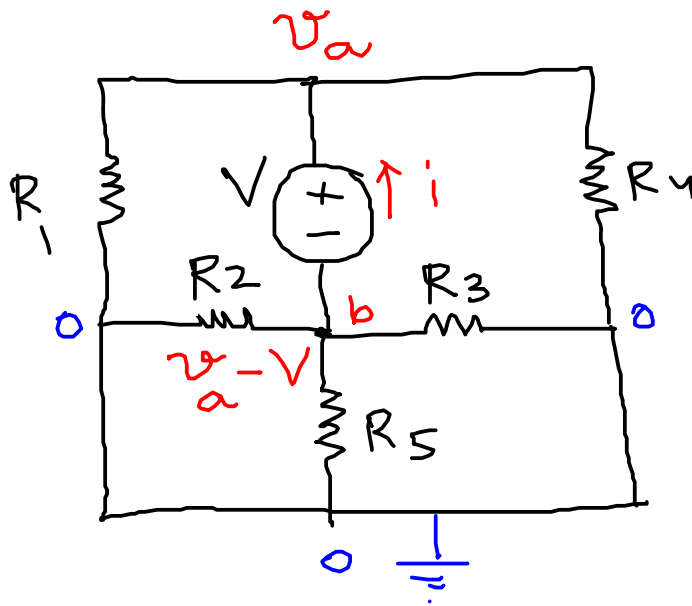

$$a: \frac{0 - v_a}{R_1} + i + \frac{0 - v_a}{R_4} = 0$$


$$b: -i + \frac{0 - v_a + V}{R_2} + \frac{0 - v_a + V}{R_5} + \frac{0 - v_a + V}{R_3}$$

Mesh Current Analysis

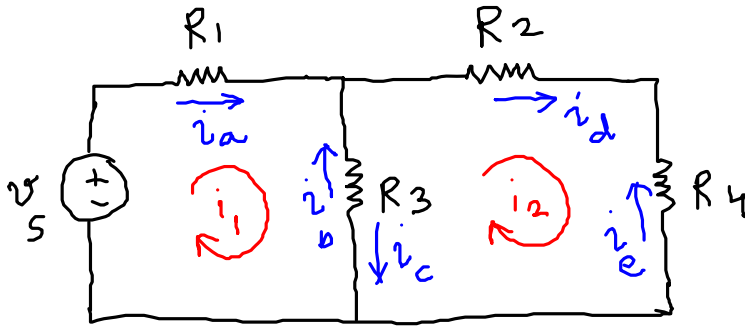


$$i_a = i_1 \quad i_b = i_2 - i_1 \quad i_c = i_1 - i_2$$

$$i_d = i_2 \quad i_e = -i_2$$

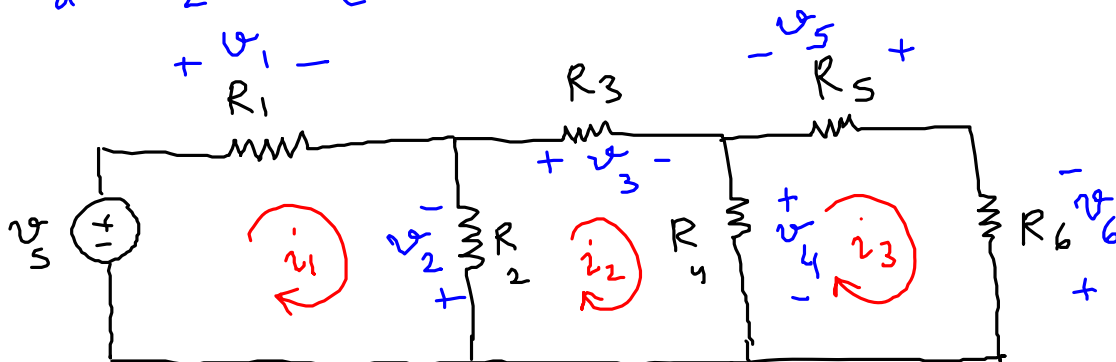

$$v_1 = i_1 R_1 \quad v_2 = (i_2 - i_1) R_2 \quad v_3 = i_2 R_3$$
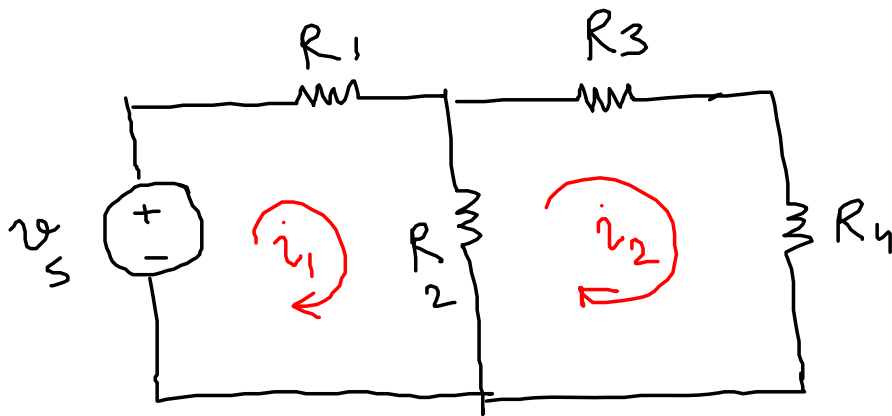
$$v_5 = -i_3 R_5 \quad v_4 = (i_2 - i_3) R_4 \quad v_6 = -i_3 R_6$$




$$\text{KVL: } i_1 \quad -v_s + R_1 i_1 + R_2 (i_1 - i_2) = 0$$

$$R_3 i_2 + R_4 i_2 + R_2 (i_2 - i_1) = 0$$


$$(R_1 + R_2) i_1 - R_2 i_2 = v_s$$

$$-R_2 i_1 + (R_2 + R_3 + R_4) i_2 = 0$$

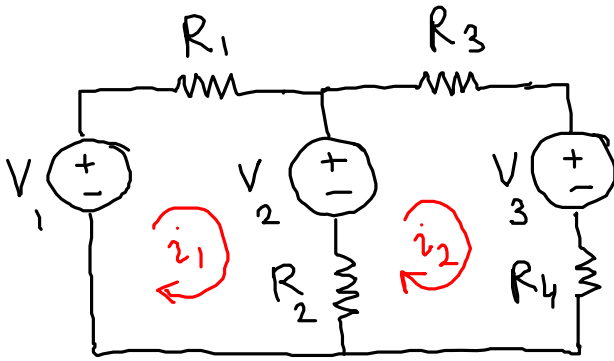

$$\text{Mesh } i_1: -V_1 + R_1 i_1 + V_2 + R_2 (i_1 - i_2) = 0$$
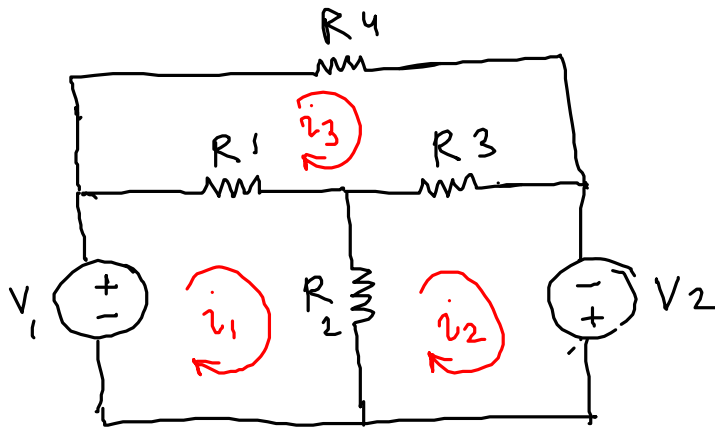
$$\text{Mesh } i_2: -V_2 + R_3 i_2 + V_3 + R_4 i_2 + R_2 (i_2 - i_1) = 0$$




$$\text{Mesh } i_1: -V_1 + R_1 (i_1 - i_3) + R_2 (i_1 - i_2) = 0$$

$$\text{Mesh } i_2: -V_2 + R_2 (i_2 - i_1) + R_3 (i_2 - i_3) = 0$$

$$\text{Mesh } i_3: R_4 i_3 + R_3 (i_3 - i_2) + R_1 (i_3 - i_1) = 0$$

Mesh Analysis with current sources

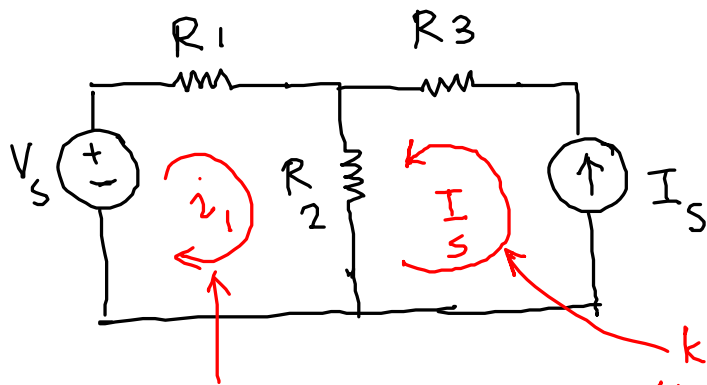


unknown mesh current
(always anticlockwise)

known mesh current
(in the direction of
the current source)

$$\text{Mesh } i_1: -V_s + R_1 i_1 + R_2 (i_1 + I_s) = 0$$

I_s is known, no need to write
a mesh equation for I_s

one equation in
one unknown

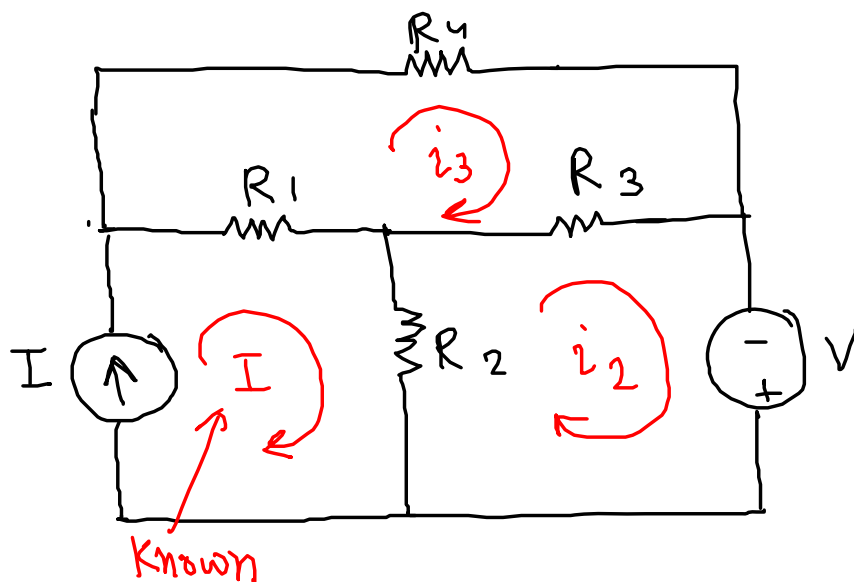

$$\text{Mesh } i_2: -V + R_2(i_2 - I) + R_3(i_2 - i_3) = 0$$


$$\text{Mesh } i_3: R_1(i_3 - I) + R_4 i_3 + R_3(i_3 - i_2) = 0$$

two equations in two unknowns

$$\text{Unknown mesh currents} = m - n$$


\swarrow
 # of meshes

\downarrow
 # of current sources

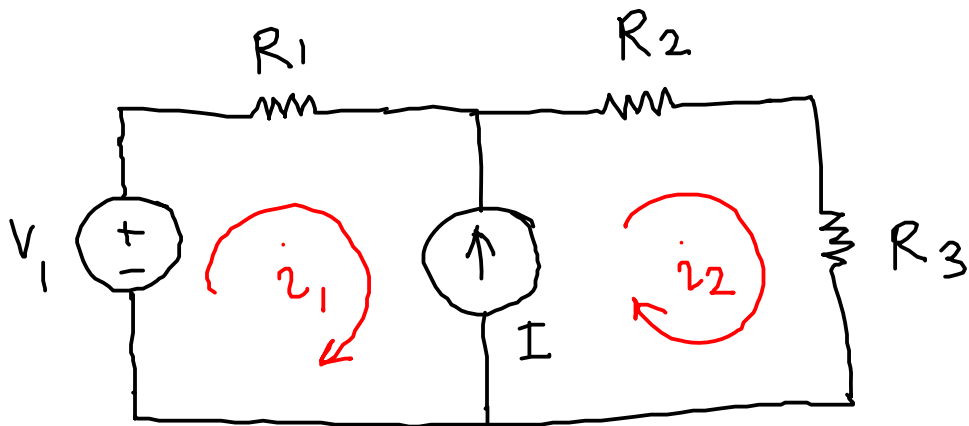

$$I = i_2 - i_1$$


$$i_2 = I + i_1$$

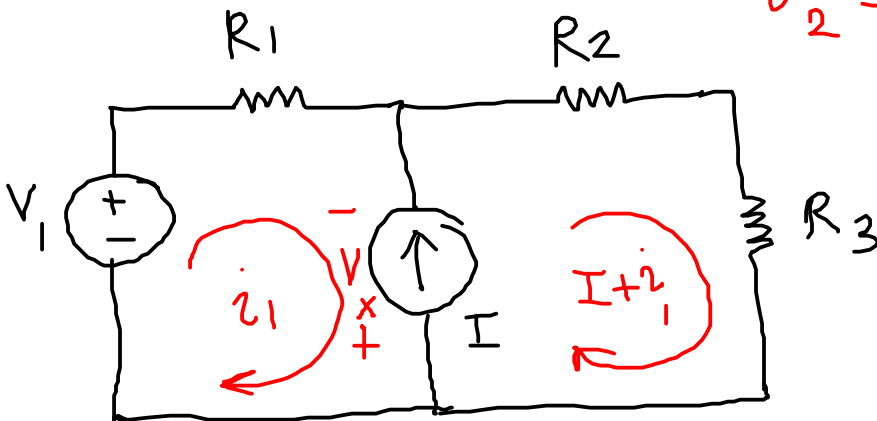


Mesh i_1 : $-V_1 + R_1 i_1 - V_x = 0$

$$+V_x + R_2 (I + i_1) + R_3 (I + i_1) = 0$$

one equation in one unknown

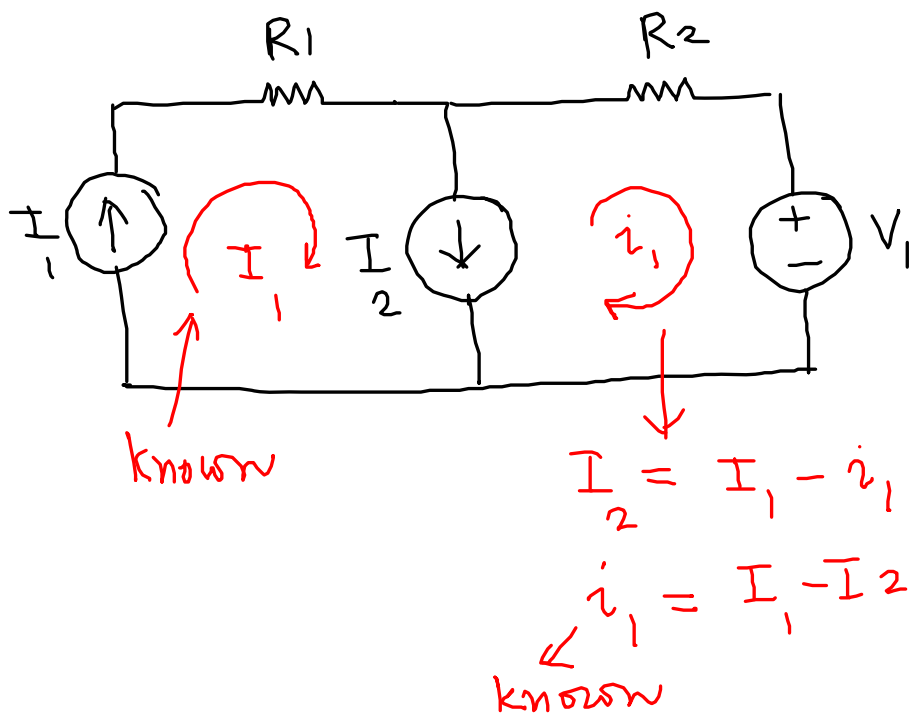

problem is already solved

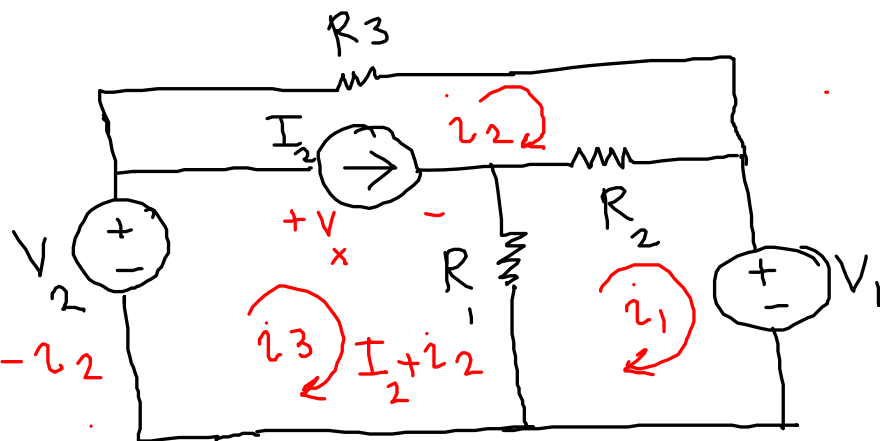

$$I_2 = i_3 - i_2$$


$$i_3 = I_2 + i_2$$

$$i_1: V_1 + R_1(i_1 - I_2 - i_2) + R_2(i_1 - i_2) = 0$$

$$i_2: -V_x + R_3 i_2 + R_2(i_2 - i_1) = 0$$

$$V_x + R_1(I_2 + i_2 - i_1) - V_2 = 0$$

Prob.

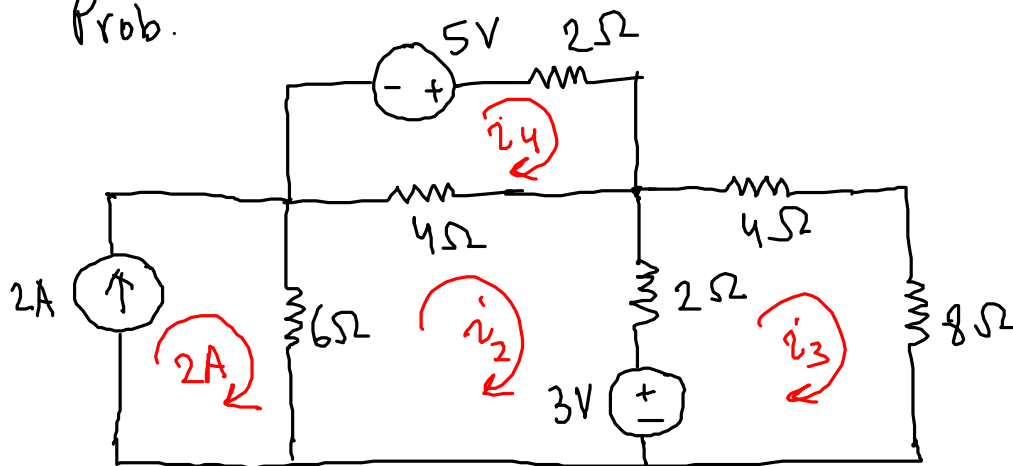


$$i_2: 6\Omega(i_2 - 2A) + 4\Omega(i_2 - i_4) + 2\Omega(i_2 - i_3) + 3V = 0$$

$$i_3: -3V + 2(i_3 - i_2) + 4\Omega i_3 + 8\Omega i_3 = 0$$

$$i_4: -5V + 2\Omega i_4 + 4\Omega(i_4 - i_2) = 0$$

3 equations, 3 unknowns

Problem

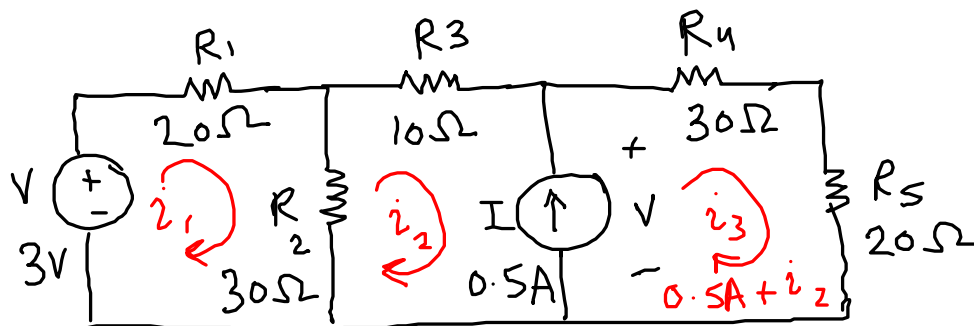find V

$$0.5A = i_3 - i_2$$

$$i_3 = 0.5A + i_2$$

$$i_1: -3V + 20\Omega i_1 + 30\Omega (i_1 - i_2) = 0$$

$$i_2: V + 30\Omega (i_2 - i_1) + 10\Omega i_2 = 0$$

$$-V + 30\Omega (0.5A + i_2) + 20\Omega (0.5A + i_2) = 0$$

two equations in two unknowns