
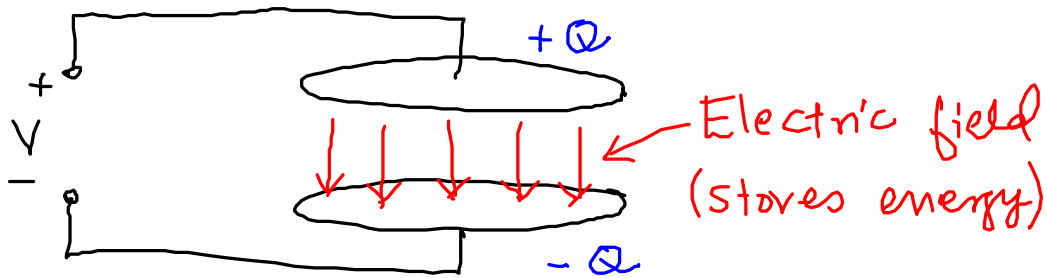


Capacitor

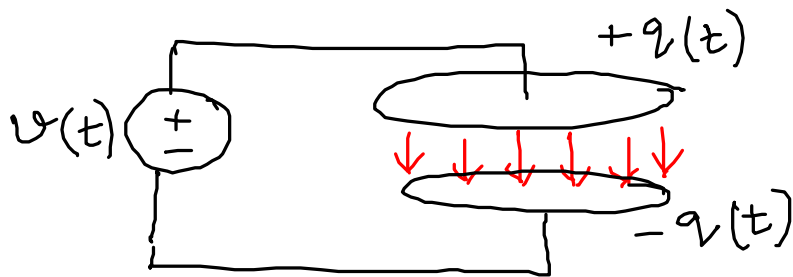


$$Q = VC$$

← capacitance
 ← coulombs ← volt ← Farad (F)




$$q(t) = C v(t)$$

$$C = \frac{\epsilon A}{d}$$

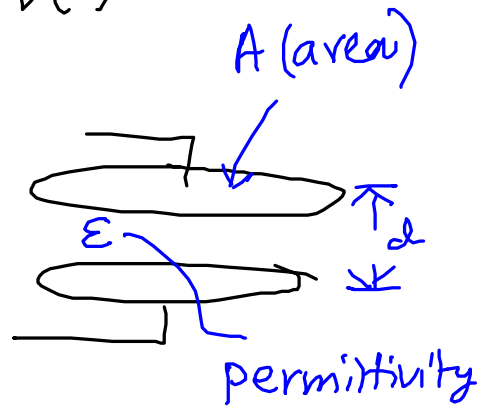

$$\epsilon = 8.854 \times 10^{-12} \text{ F/m}$$

for air

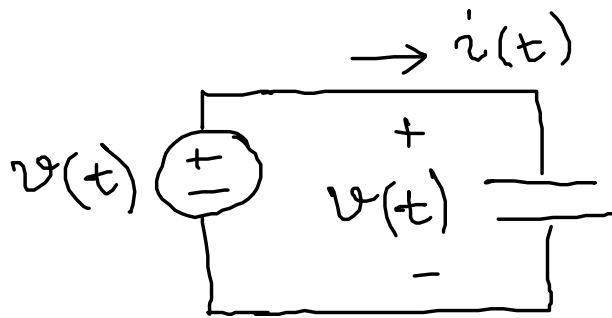

$$i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t') dt'$$

$$V_0 = v(t = t_0) = \frac{1}{C} \int_{-\infty}^{t_0} i(t') dt'$$


$$t > t_0 \rightarrow v(t) = V_0 + \frac{1}{C} \int_{t_0}^t i(t') dt'$$

typically $t = 0$

$$t \geq 0 \rightarrow v(t) = V_0 + \frac{1}{C} \int_0^t i(t') dt'$$


voltage across the capacitor at $t = 0$

series capacitors

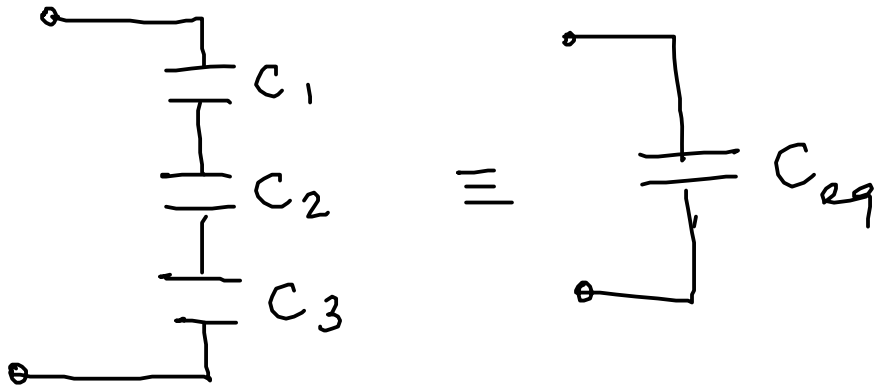


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

parallel capacitors

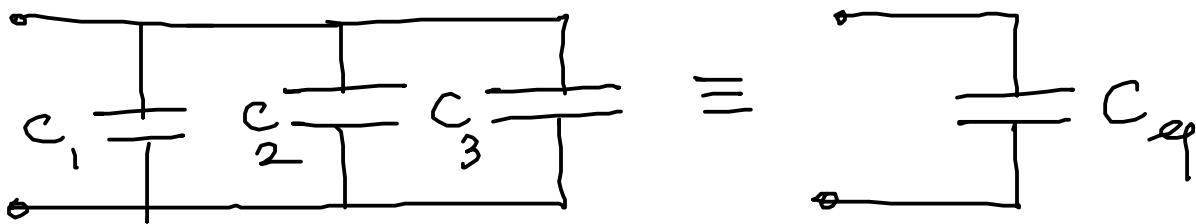

$$C_{eq} = C_1 + C_2 + C_3$$

Examples

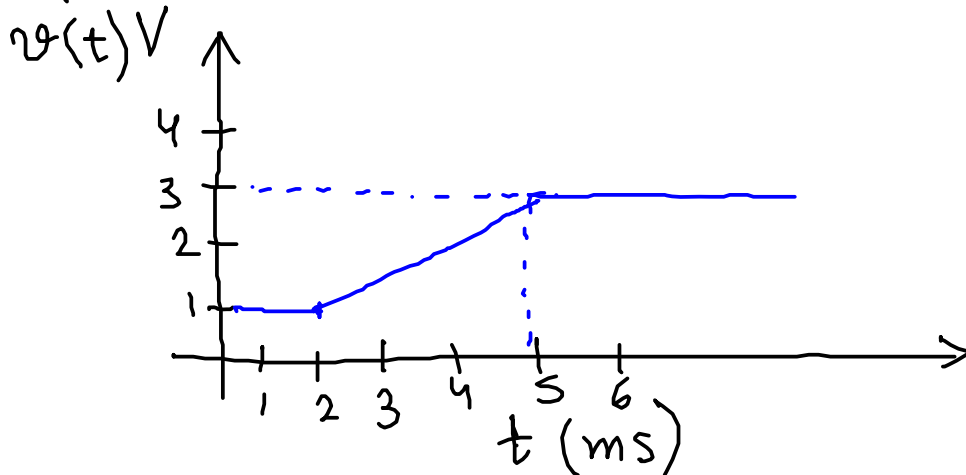

$$C = 1000 \mu\text{F}$$

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = 0 \quad \text{for } 0 < t < 2 \text{ ms}$$

$$i(t) = (1000 \mu\text{F}) \left(\frac{2\text{V}}{3 \text{ ms}} \right)$$


$$= 1000 \times 10^{-6} \text{ F} \frac{2\text{V}}{3 \times 10^{-3} \text{ s}}$$

$$= \frac{2}{3} \text{ A} \quad \text{for } 2 \text{ ms} < t < 5 \text{ ms}$$

$$i(t) = 0 \quad \text{for } t > 5 \text{ ms}$$



Example


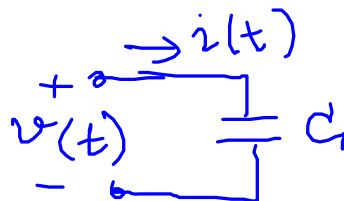


$$i(t) = \begin{cases} 10\text{mA} & 0 \leq t \leq 1\text{s} \\ 0 & t > 1\text{s} \end{cases} \quad C = 1000\mu\text{F}$$

$$V_0 = v(t=0) = 2\text{V}$$

$$v(t) = V_0 + \frac{1}{C} \int_0^t i(t') dt'$$

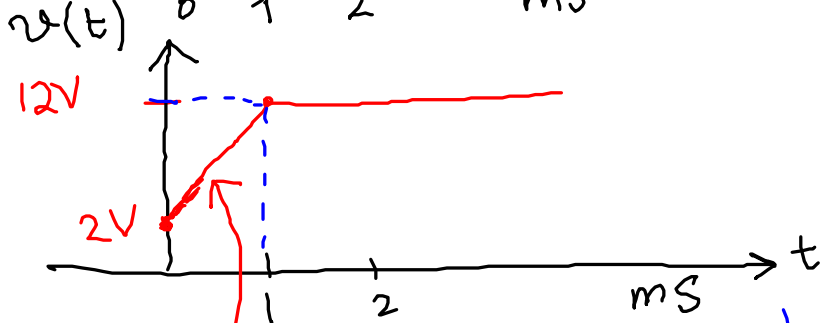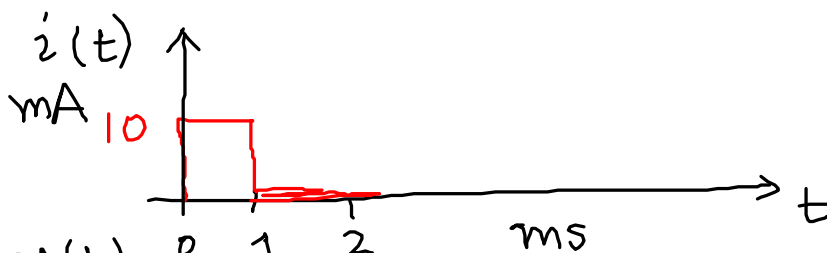(Note: A handwritten "2V" is written above the V_0 term in the original image.)



$0 \leq t < 1 \text{ ms}$


$$v(t) = 2\text{V} + \frac{1}{10^{-3}\text{F}} \int_0^t 10\text{mA} dt'$$

$$= 2\text{V} + 10t$$


(A red bracket is drawn under the $2\text{V} + 10t$ result.)

Energy stored in a capacitor

$$W_C(t) = \frac{1}{2} C v^2(t)$$

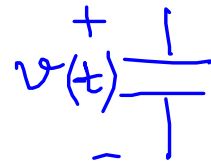

Inductor

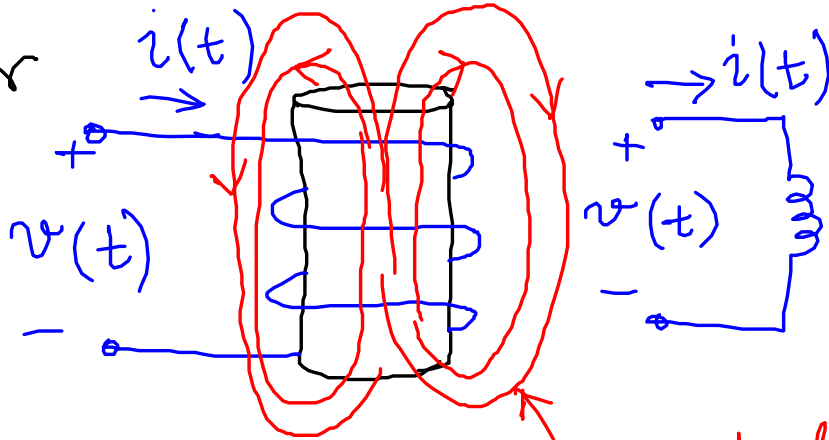

Magnetic field (stores energy)

$$v(t) = L \frac{di(t)}{dt}$$


inductance (H) henrys

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t') dt'$$


$$I_0 = i(t = t_0)$$

$$i(t) = I_0 + \frac{1}{L} \int_{t_0}^t v(t') dt' \quad t > t_0$$


Inductors in series

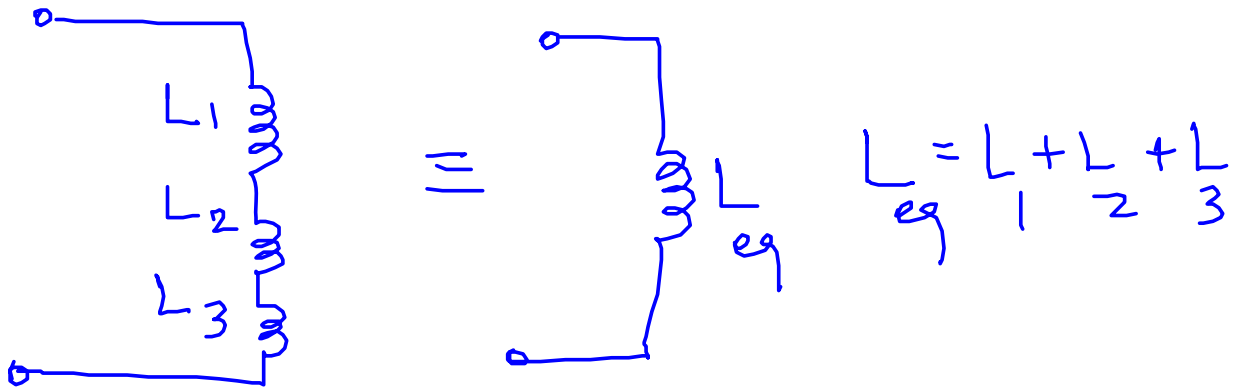

Inductors in parallel

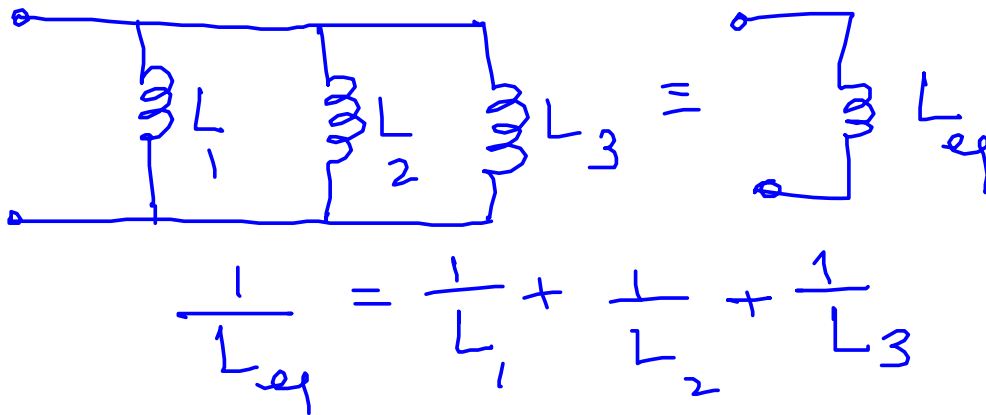




Time dependent signal sources

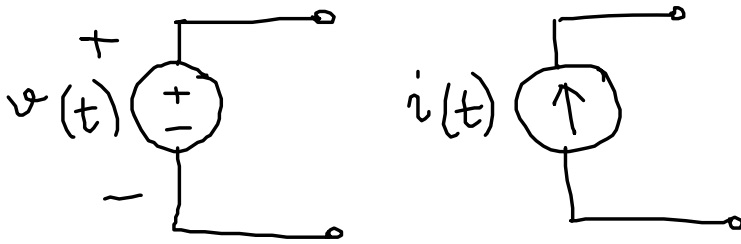

periodic signals

$$x(t) = x(t + nT) \quad n=1, 2, 3, \dots$$

↗ period

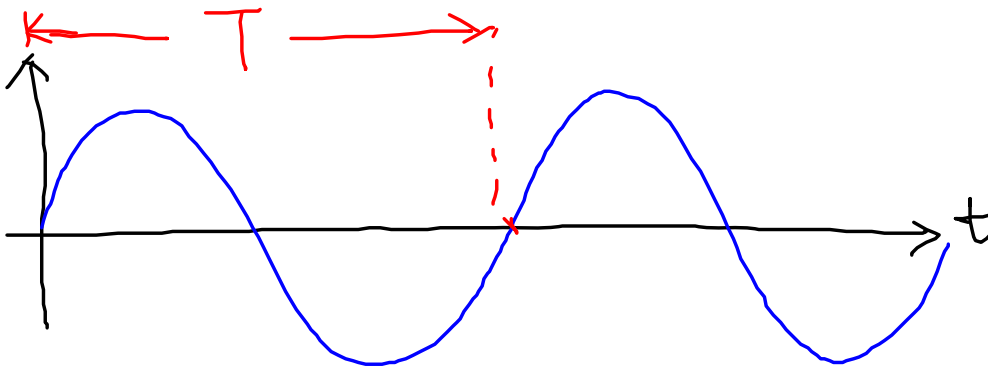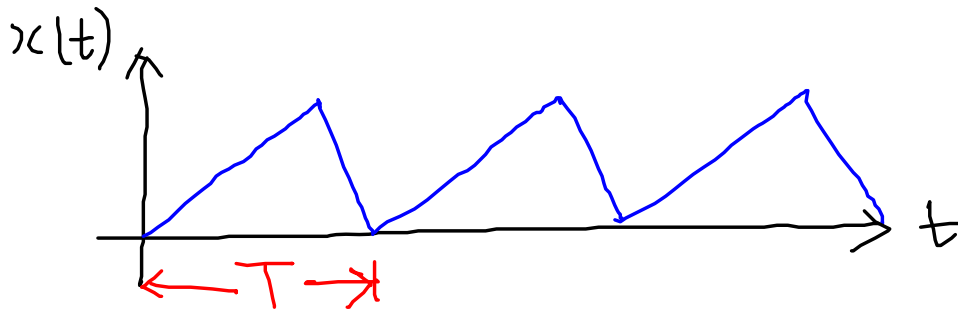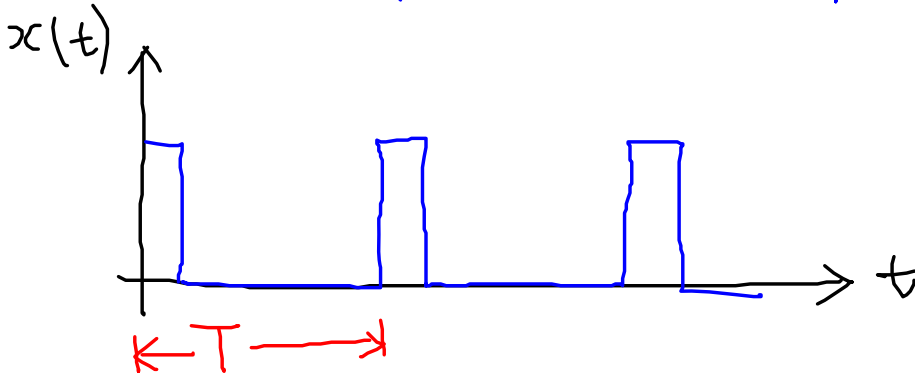


sinusoidal wave forms

$$x(t) = A \cos(\omega t + \phi)$$

Amplitude (V or A) \swarrow
 angular (radian) frequency rad/sec \swarrow
 phase (radians or degrees) \nearrow

Note $A \sin(\omega t) = A \cos(\omega t - \frac{\pi}{2})$

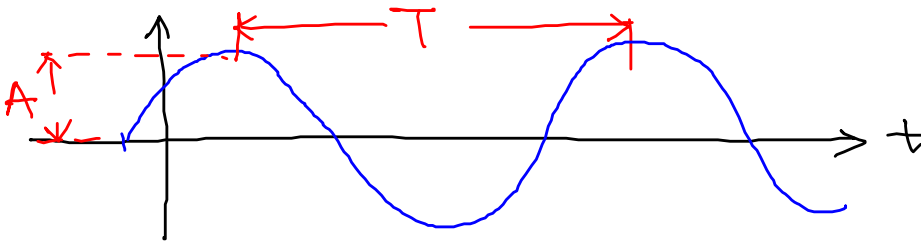$A \cos(\omega t) = A \sin(\omega t + \frac{\pi}{2})$



frequency cycles/sec \rightarrow hertz (Hz)

$\omega = 2\pi f$
 \nearrow
 radial frequency
 (rad/sec)

$f = \frac{1}{T}$
 \nearrow
 natural frequency
 (cycles/sec, Hz)

$$T = \frac{1}{f}$$

$$T = \frac{2\pi}{\omega}$$